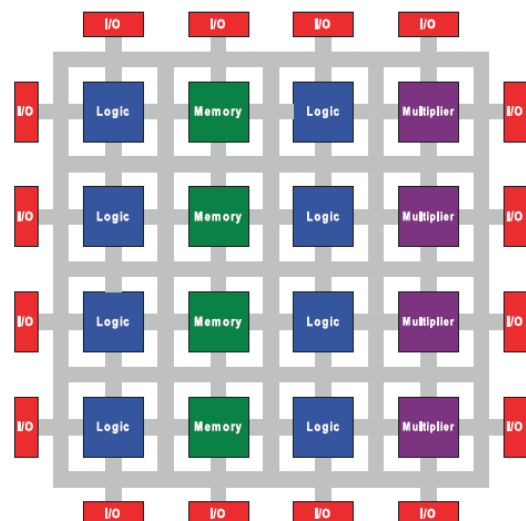


Classification and Evolution of Field Programmable Logic Devices

1


Topics

- Distinction from ASIC
- Classification & evolution of FPLDs
- FPLD markets



2

Field-Programmable Gate Array (FPGA)

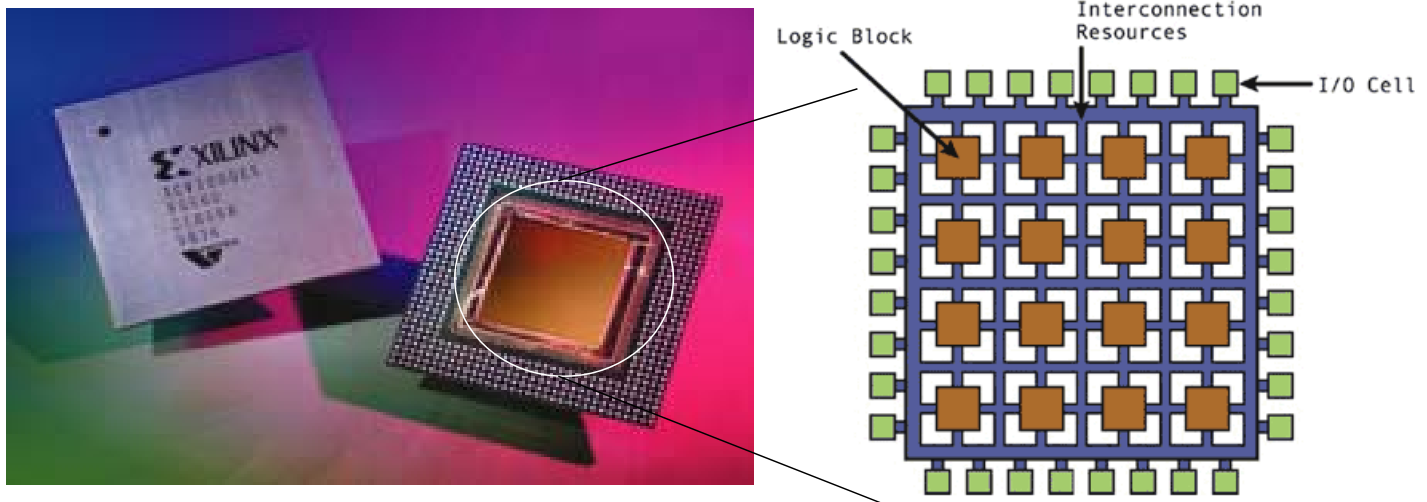

3

Field-Programmable Devices


- *User-configurable* ICs.
- They are standard parts, not designed for any particular application.
- Unlike traditional ASIC, logic function is specified by the user *after* the device is manufactured.
- They are programmed/configured by the users to implement their designs *at their own sites*.
- *Instant configuration* (in minutes) at users' site.



4

Advantages of Field-Programmable Logic Devices

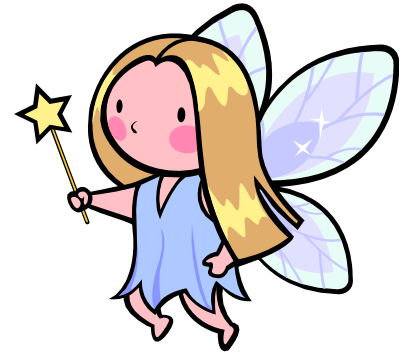- Short turnaround time for new designs
- Low startup cost
- Low inventory cost
- Low risk
- Allow easy design changes



5

How to make a chip that can realize different circuits and configurable?

What are the essential elements that make up any circuit?

6

What do you expect within a FPLD?

大量的

1. Substantial amounts of uncommitted combinational logic.
2. Contain flip-flops/latches.
3. Programmable interconnections between the combinational logic, flip-flops, and chip input/outputs.

7

Types of Field-Programmable Devices

- *Simple Programmable Logic Devices (SPLDs)*
- *Complex Programmable Logic Devices (CPLDs)*
- *Field-Programmable Gate Arrays (FPGAs)*


8

Programmable Logic Array (PLA)

- A simple programmable logic device (SPLD).
- The first programmable logic device introduced in the early 1970s by Philips.
- Use a *2-level logic* structure to implement programmed logic.
- Based on idea that logic functions can be realized in *sum-of-products* form.
- A programmable array of AND gates feeding a programmable array of OR gates.


9

PLA Structure

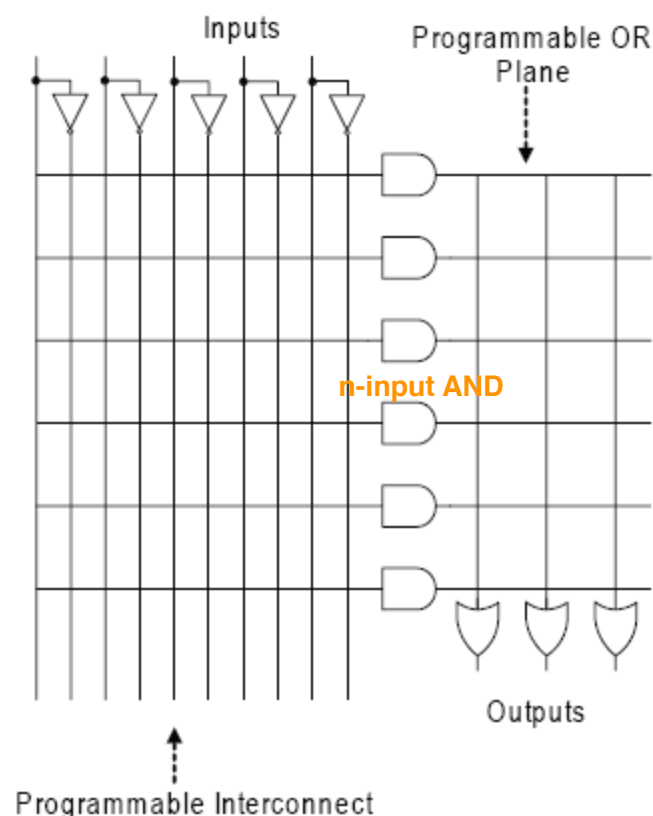

10

Function Implementation by PLA

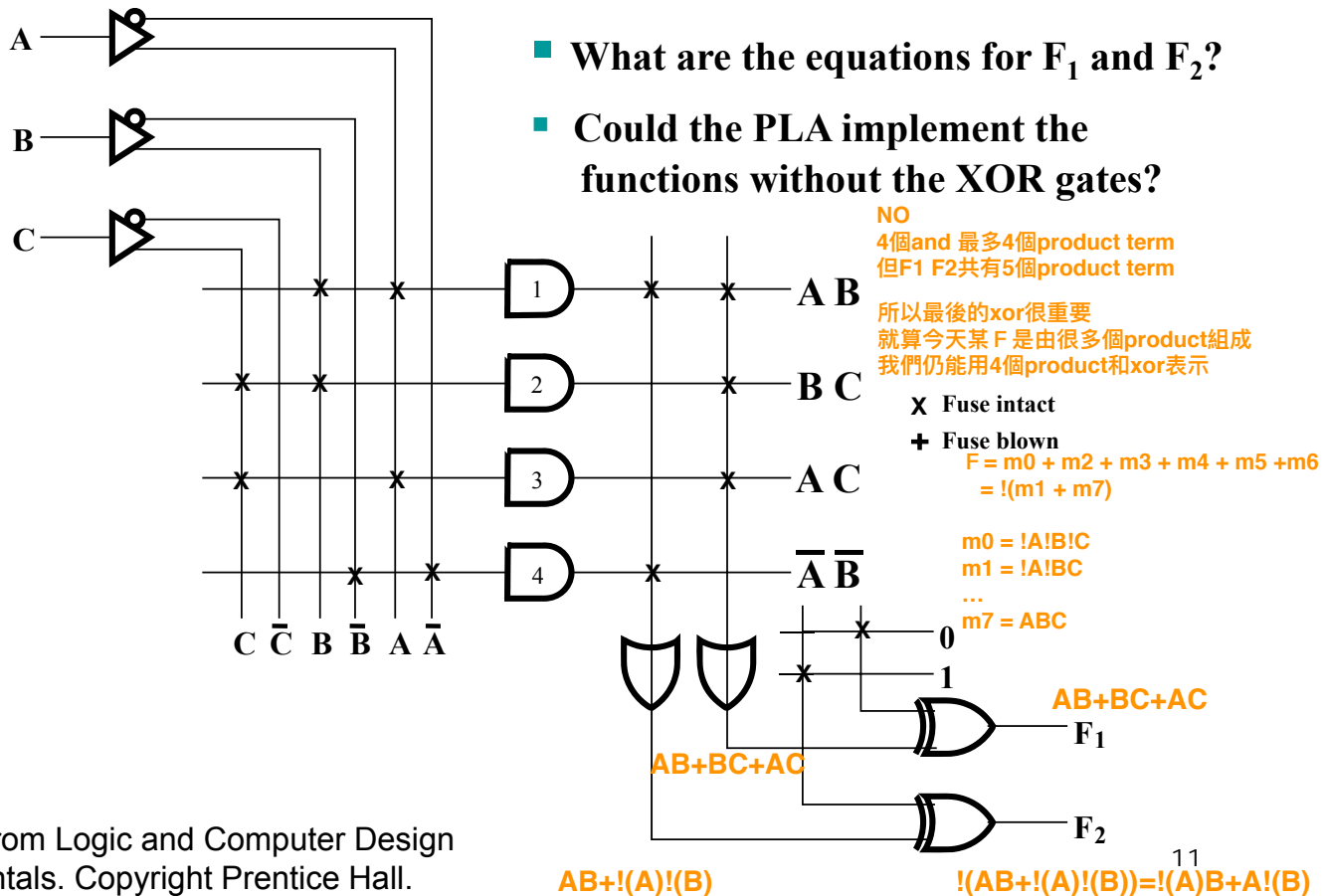


Adapted from Logic and Computer Design Fundamentals. Copyright Prentice Hall.

Programmable Array Logic (PAL)

- Introduced to overcome the weaknesses of PLAs (programmable switches were hard to fabricate correctly and introduced significant propagation delays).
- A programmable array of AND gates feeding a fixed array of OR gates.
- PAL usually contains flip-flops connected to the OR gate outputs to implement sequential circuits.
(Macrocell: an OR gate combined with a flip-flop and extra circuitry in a PAL.)
- PLAs and PALs are useful for implementing small digital circuits, typically ≤ 32 combined inputs and outputs.

PAL Structure

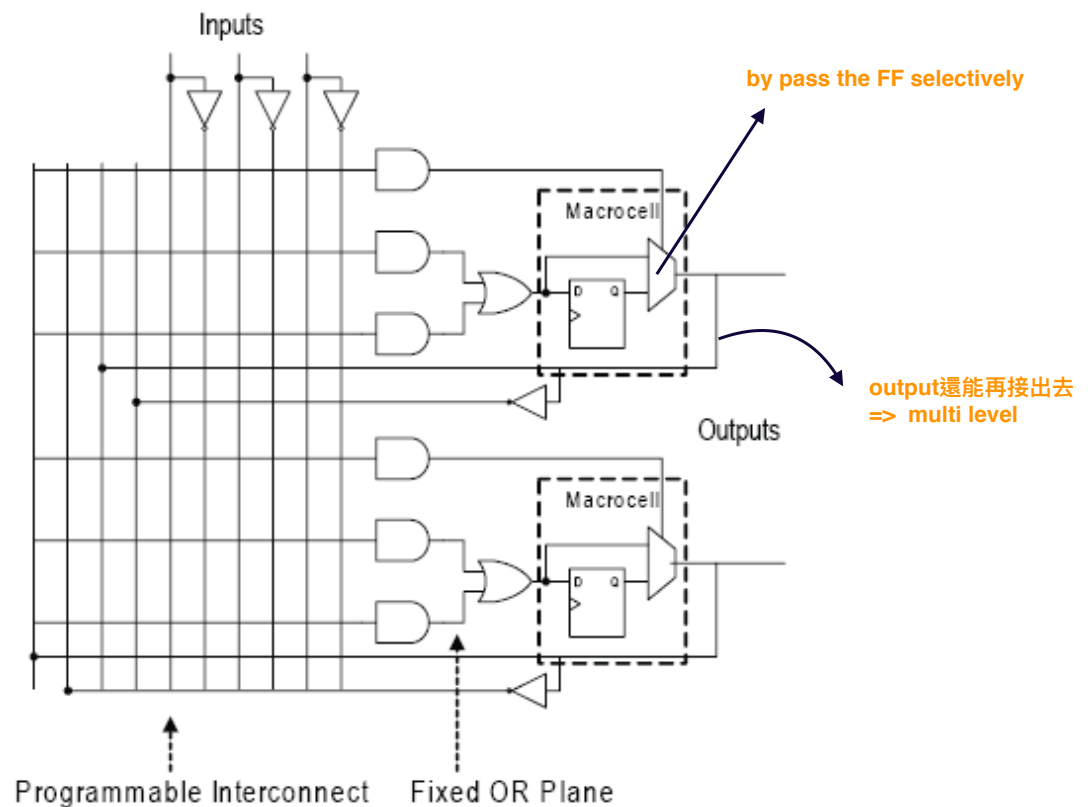

13

Function Implementation by PAL


- 4-input, 4-output PAL with fixed, 3-input OR terms
- What are the equations for F1 through F4?

$$F1 = \overline{A} \overline{B} + \overline{C}$$

$$F2 = \overline{A} B \overline{C} + AC + AB$$


$$F3 =$$

$$F4 =$$

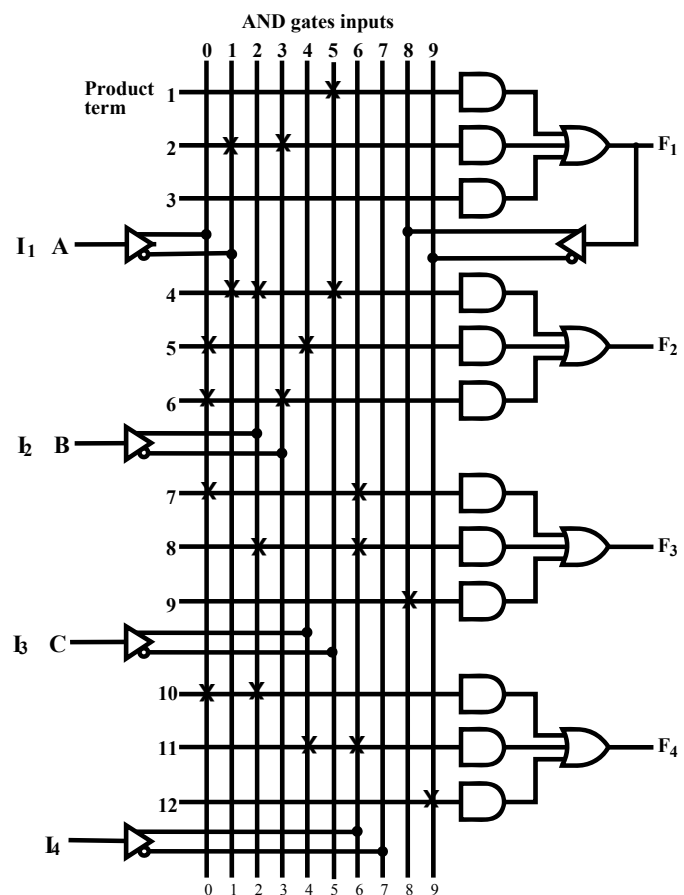


14

PAL and PLA Comparison

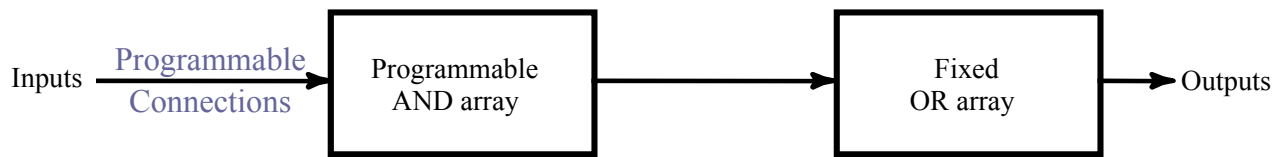

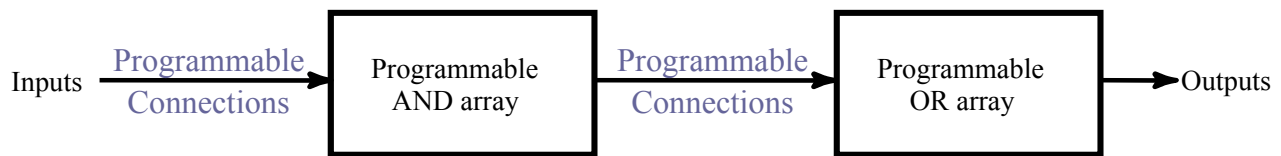(a) Programmable array logic (PAL) device



(b) Programmable logic array (PLA) device


Adapted from Logic and Computer Design
Fundamentals. Copyright Prentice Hall.

15

How to get larger capacity?

16

Complex Programmable Logic Device (CPLD)

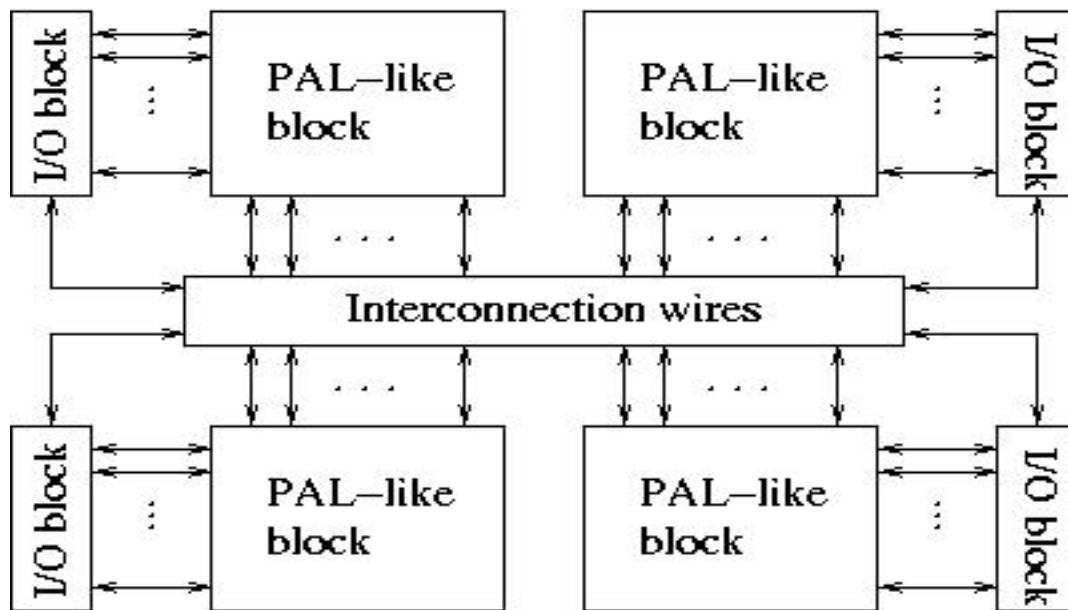

17

Complex Programmable Logic Device


- Combines multiple PAL-like blocks with programmable interconnect network.
- Provides much larger capacity than SPLDs.

basic idea for SPLD/CPLD is sum of product
but not for FPGA

18

Field-Programmable Gate Array (FPGA)

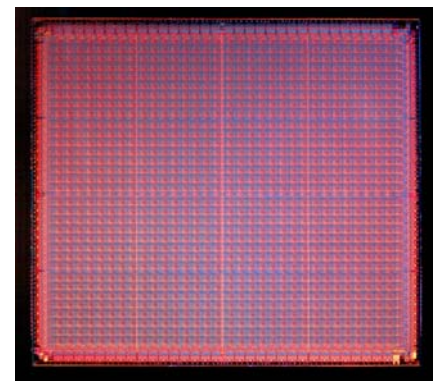
- A high-capacity programmable logic device providing multi-level logic.
- Introduced in 1985 by Xilinx.
- Classic FPGA consists of an array of programmable logic blocks surrounded by programmable interconnect.




Xilinx XC4000ex

19

Field-Programmable Gate Array

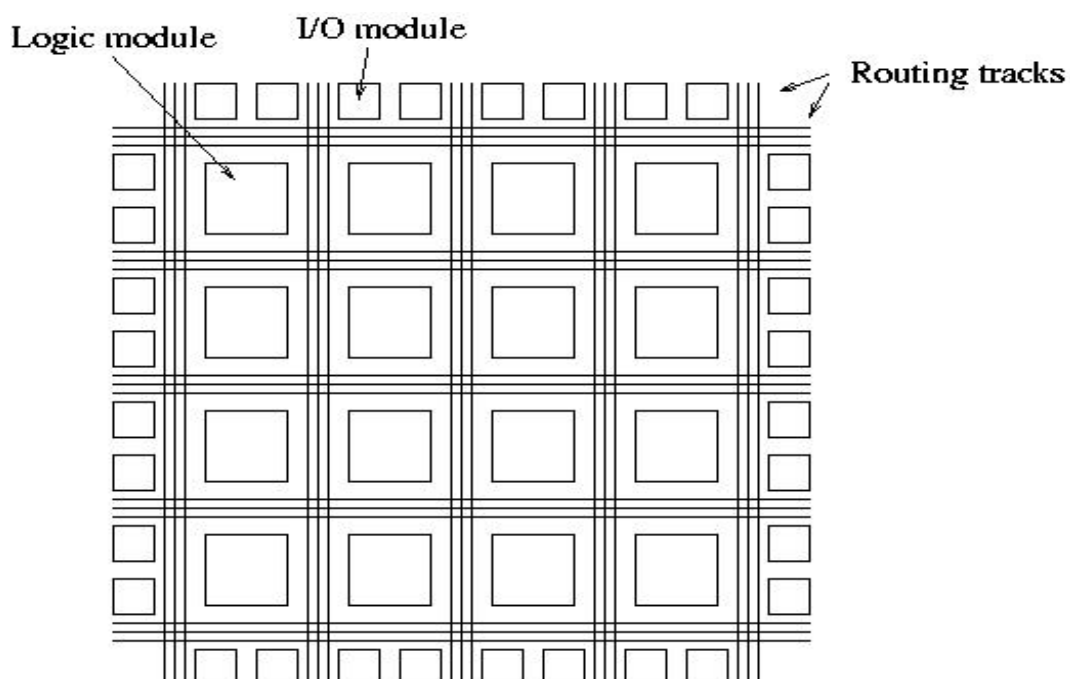


SRAM-Based FPGA

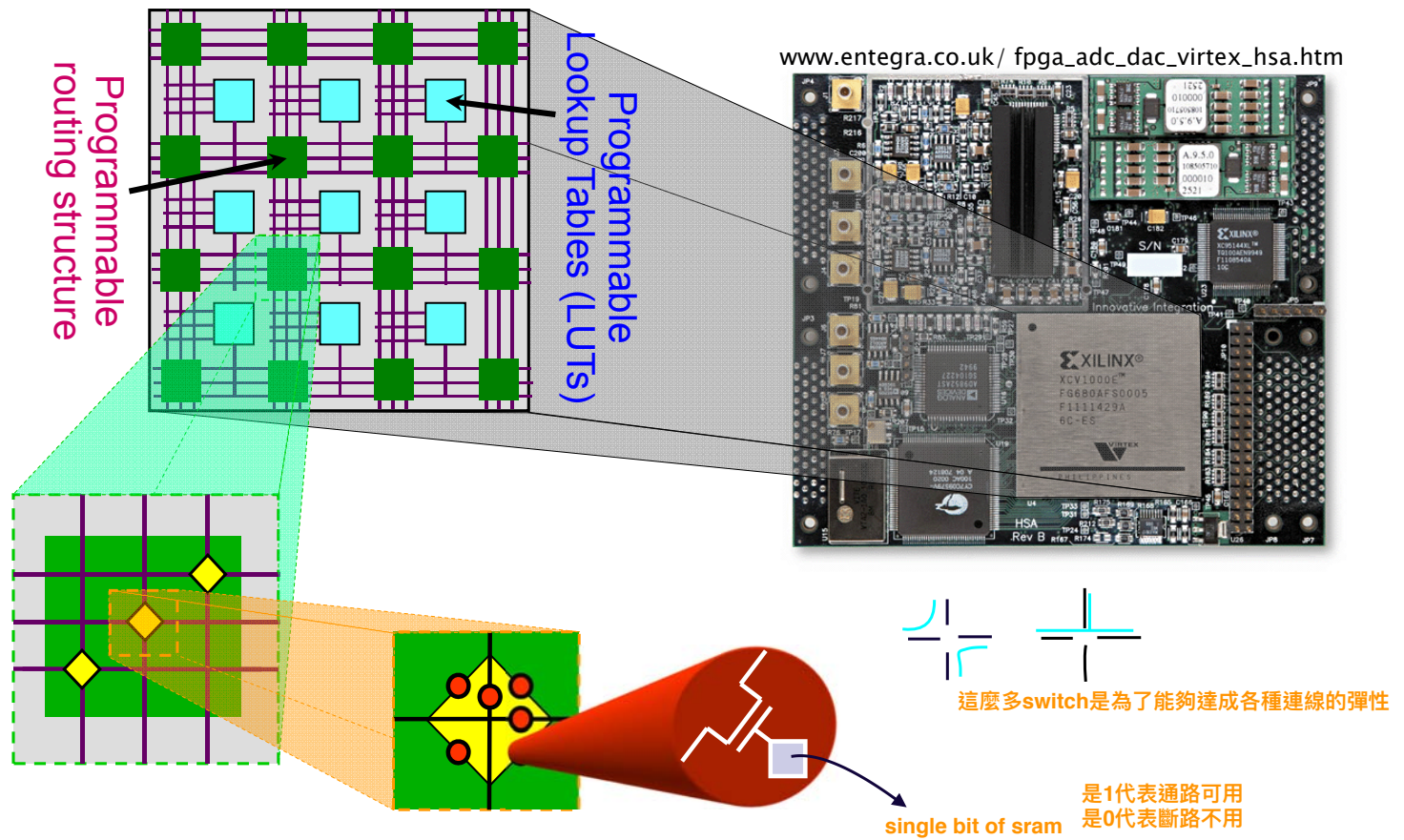

K. Bazargan²¹

SRAM-Based FPGA

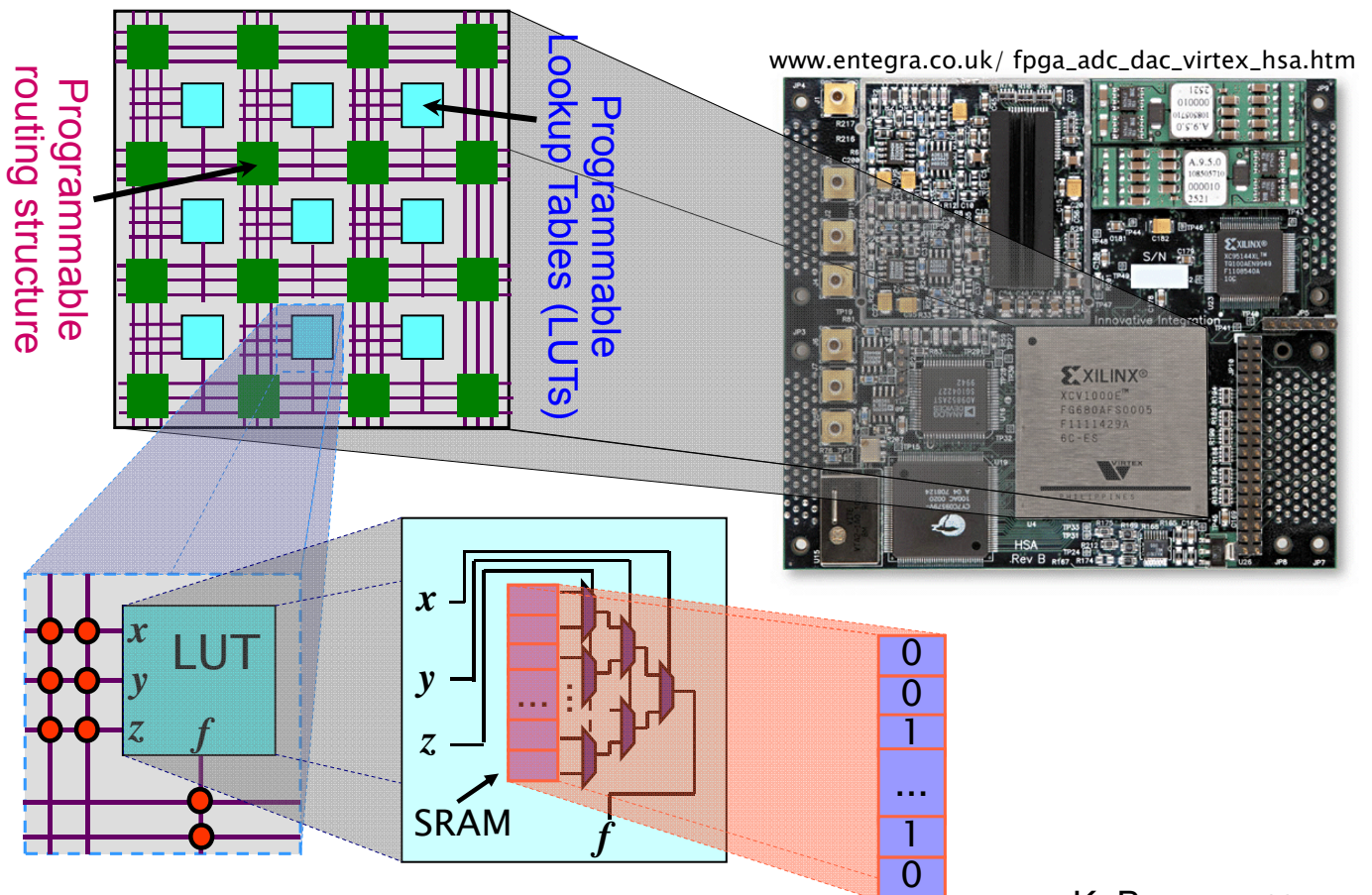

K. Bazargan²²

Microprocessor vs Custom Chip vs FPGA

ie. ASIC

■ Microprocessor

- ☐ Rely on software to implement functions
- ☐ Slowest, most power-hungry
- ☐ Re-programmable (load different software)

■ Custom Chip

- ☐ Designed for a particular purpose
- ☐ Fastest, most power-efficient
- ☐ Not re-programmable

■ FPGA

- ☐ Not designed for any particular function
- ☐ In between microprocessor and custom chip in speed and power
- ☐ Re-programmable (most)

23

Rapidly Increasing Logic Capacity

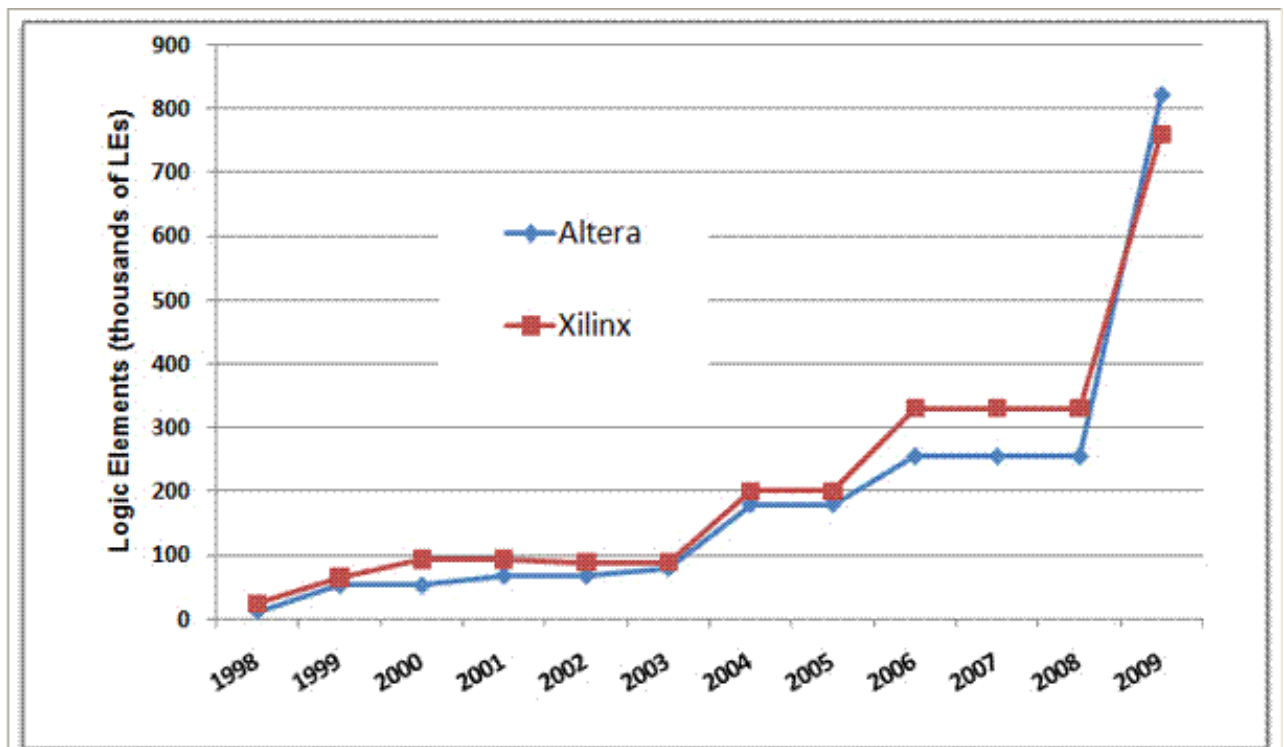


Figure 1. Largest FPGA announced (by equivalent 4-input Logic Elements - LEs).


24

Today's FPGAs

- Additional resources: embedded memory blocks, fast carry logic chains, DSP blocks
- Versatile programmable I/Os
- Some even contain: 1 or more processors
- Applications: audio, video, wireless, industrial equipments, network components, medical, automotive, etc.
- Vendors offer a variety of FPGAs catering for different markets


25

Advanced Features of Today's FPGAs

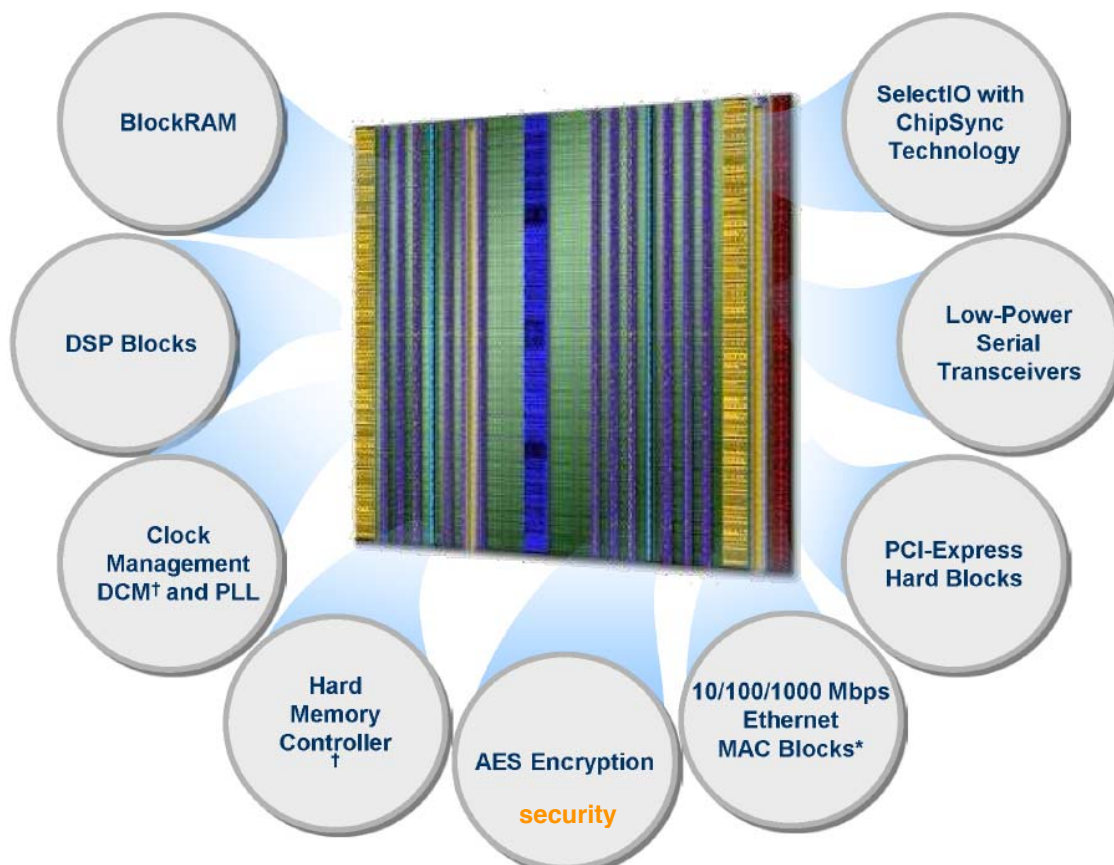

26


Advanced Features of Today's FPGAs

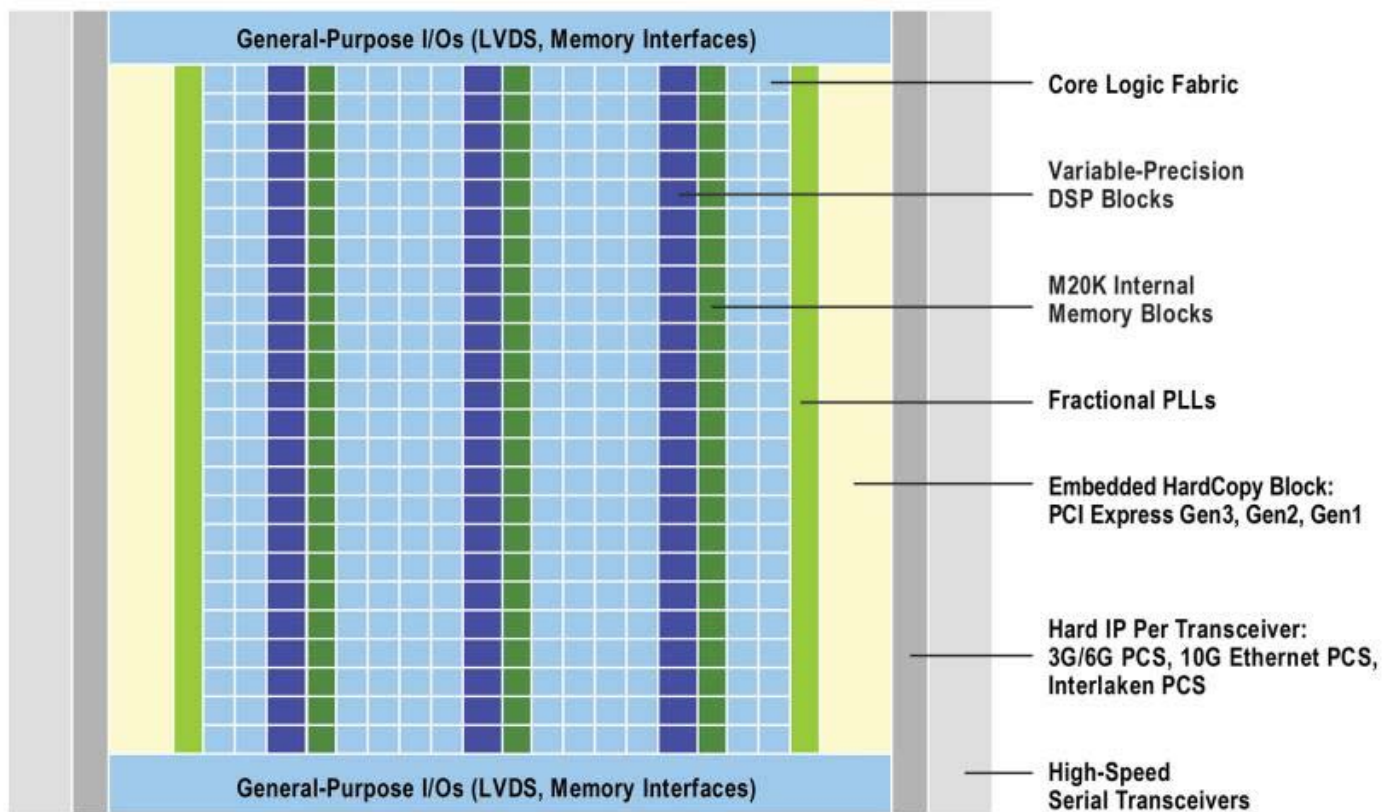

2 /

SoC FPGA

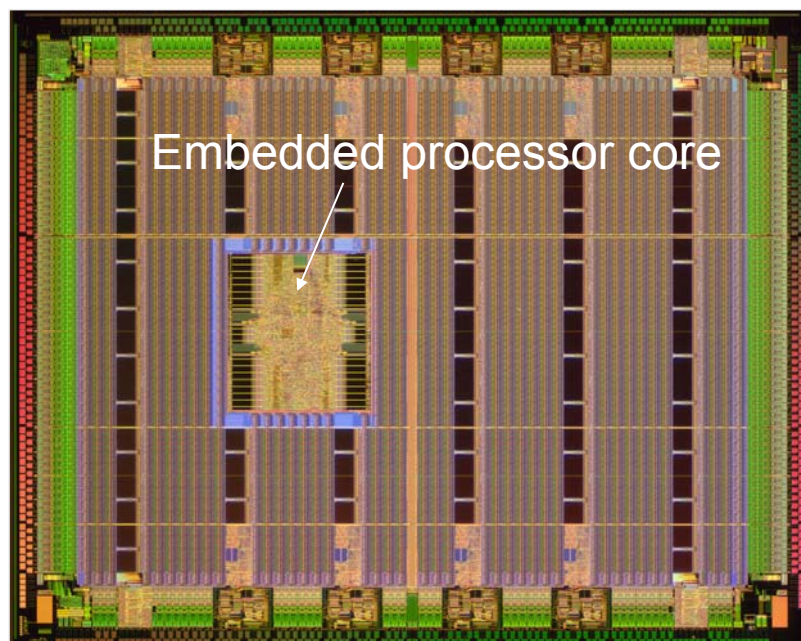- Xilinx's Zynq families and Intel's SoC FPGAs
 - with 1 or more ARM cores



28